

Circuits and Electronics

Name: MD. Abdul Kahhar Siddiki Shan

ID: 18301221

Course code: CSE250

Section: 14

Experiment no: 02

Experiment name: Introduction to series
and parallel circuits.

Date of Submission: 21st November, 2020

2 (1)

Name of the Experiment:

Introduction to series and parallel circuits.

Objective:


The experiment is to acquaint the students with series-parallel circuits and to give them the idea about how to connect different circuits in bread board.

Apparatus:


- i) DC power supplies
- ii) Resistors
- iii) Bread board / Trainer board
- iv) Multimeter

2(2)

Circuit / Block / System Diagram:

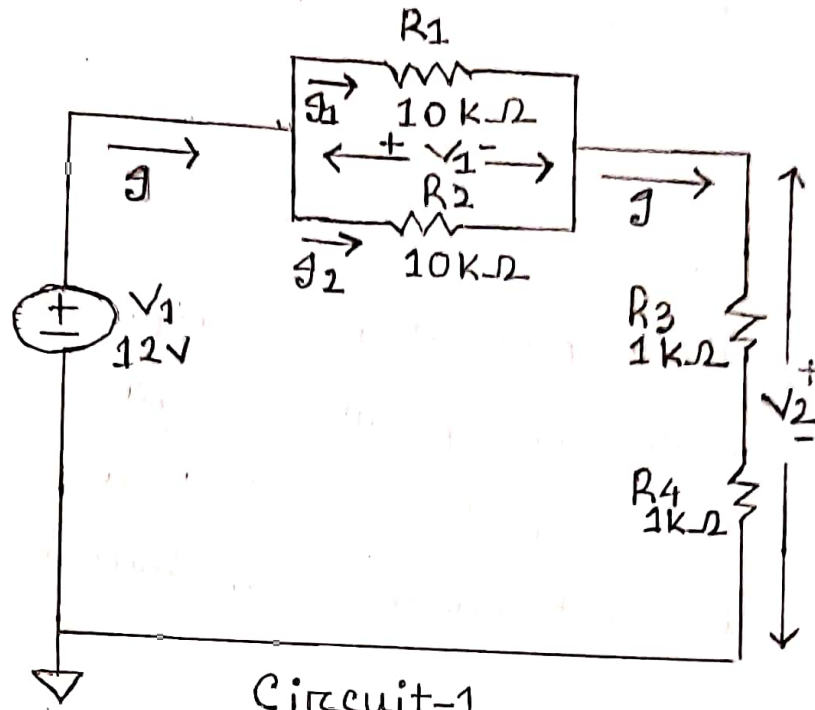

Circuit-1

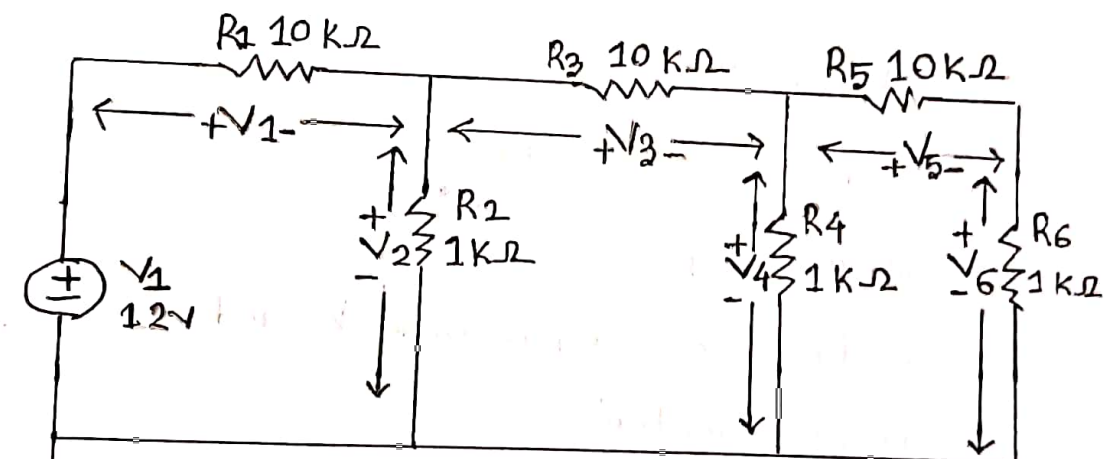

Circuit-2

3(1)

Result/Analysis:Circuit-1:

In Circuit-1, there are four resistors and they are R_1 , R_2 , R_3 and R_4 . Here, R_1 and R_2 are connected in parallel. On the other hand, R_3 and R_4 are connected in parallel. The voltage and current of each resistors are given below:

$$\text{Here, } V = 12 \text{ V}$$

$$R_1 = R_2 = 10 \text{ K}\Omega$$

$$R_3 = R_4 = 1 \text{ K}\Omega$$

$$\therefore \frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\begin{aligned} \Rightarrow R_{12} &= \frac{R_1 \times R_2}{R_2 + R_1} = \left(\frac{10 \times 10}{10 + 10} \right) \text{ K}\Omega \\ &= \left(\frac{100}{20} \right) \text{ K}\Omega \\ &= 5 \text{ K}\Omega = 5000 \Omega \end{aligned}$$

Again,

$$\begin{aligned} R_{34} &= R_3 + R_4 \\ &= (1 + 1) \text{ K}\Omega = 2 \text{ K}\Omega = 2000 \Omega \end{aligned}$$

3(2)

$$\begin{aligned}\text{Total resistance } R &= R_{12} + R_{34} \\ &= (5000 + 2000) \Omega \\ &= 7000 \Omega\end{aligned}$$

$$\begin{aligned}\text{Total current } I &= \frac{V}{R} \\ &= \frac{12}{7000} \\ &= 1.71428 \times 10^{-3} \text{ A} \\ &= 1.714 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{Voltage } V_1 &= IR_{12} \\ &= (1.714 \times 5000) \text{ mV} \\ &= 8570 \text{ mV} \\ &= 8.57 \text{ V}\end{aligned}$$

Here voltage V_1 for R_1 and R_2 resistors. As they are connected in parallel, their voltage will be same.

4 (1)

$$\begin{aligned}\text{Voltage } V_2 &= I R_{34} \\ &= (1.714 \times 2000) \text{ mV} \\ &= 3428 \text{ mV} \\ &= 3.428 \text{ V}\end{aligned}$$

$$\begin{aligned}I_1 &= \frac{V_1}{R_1} = \frac{8.57}{10 \times 10^3} = 0.857 \\ &= 8.57 \times 10^{-4} \text{ A} \\ &= 857 \text{ } \mu\text{A}\end{aligned}$$

$$\begin{aligned}I_2 &= \frac{V_1}{R_2} = \frac{8.57}{10 \times 10^3} \\ &= 8.57 \times 10^{-4} \text{ A} \\ &= 857 \text{ } \mu\text{A}\end{aligned}$$

Here R_3 & R_4 are connected in series. In series connection, the current flow will be same. So, there current flow is $I = I_3 = I_4$.

$$\therefore I = I_3 = I_4 = 1.714 \text{ mA}$$

4(2)

However, In series connection, voltage will not be same. So, the voltage of R_3 and R_4 are given below:

Voltage of R_3

$$\begin{aligned} V_3 &= I R_3 \\ &= (1.714 \times 1000 \times 10^{-3}) \text{ V} \\ &= 1.714 \text{ V} \end{aligned}$$

Voltage of R_4

$$\begin{aligned} V_4 &= (1.714 \times 10^{-3} \times 1 \times 10^3) \text{ V} \\ &= 1.714 \text{ V} \end{aligned}$$

$$V_5 = V_3 = V_4 = 1.714 \text{ V}$$

The hand calculation and the results using PSpice simulation are given below:

	Theoretical calculation	PSpice Simulation result
V	12 V	12 V
V_1	8.57 V	8.571 V
V_2	3.428 V	3.429 V
$V_5 = V_3 = V_4$	1.714 V	1.714 V
I	1.714 mA	1.714 mA
I_1	857 mA	857.14 mA
I_2	857 mA	857.14 mA
$I = I_3 = I_4$	1.714 mA	1.714 mA

5 (1)

Circuit-2:

In circuit-2, there are 6 resistors and they are R_1, R_2, R_3, R_4, R_5 and R_6 . The voltage and current of each resistor are given below:

$$V = 12 \text{ V}$$

$$R_1 = R_3 = R_5 = 10 \text{ k}\Omega = 10000 \Omega$$

$$R_2 = R_4 = R_6 = 1 \text{ k}\Omega = 1000 \Omega$$

Here, R_5 and R_6 are connected in series.

$$\begin{aligned} \therefore R_{56} &= R_5 + R_6 \\ &= (10 + 1) \text{ k}\Omega \\ &= 11 \text{ k}\Omega \end{aligned}$$

Here, R_4 and R_{56} are in parallel.

$$\begin{aligned} \therefore R_{456} &= \frac{R_{56} \times R_4}{R_4 + R_{56}} \\ &= \left(\frac{1 \times 11}{1 + 11} \right) \text{ k}\Omega \\ &= \frac{11}{12} \text{ k}\Omega \end{aligned}$$

5(2)

Now, R_3 and R_{456} are in series.

$$\begin{aligned}\therefore R_{3456} &= R_3 + R_{456} \\ &= \left(10 + \frac{112}{12}\right) \text{ k}\Omega \\ &= \left(\frac{131}{12}\right) \text{ k}\Omega\end{aligned}$$

Here, R_2 and R_{3456} are in parallel.

$$\begin{aligned}\therefore R_{23456} &= \frac{R_2 \times R_{3456}}{R_{3456} + R_2} \\ &= \left(\frac{1 \times \frac{131}{12}}{\frac{131}{12} + 1}\right) \text{ k}\Omega \\ &= \frac{131}{143} \text{ k}\Omega\end{aligned}$$

Now, R_1 and R_{23456} are connecte in series.

$$\begin{aligned}\therefore R_{123456} &= R_1 + R_{23456} \\ &= \left(10 + \frac{131}{143}\right) \text{ k}\Omega \\ &= \left(\frac{1561}{143}\right) \text{ k}\Omega \\ &= 10916.084 \Omega\end{aligned}$$

G (1)

$$\begin{aligned}\text{Total current } I &= \frac{V}{R_{23456}} \\ &= \frac{12}{10916.089} \\ &= 1.099295315 \times 10^{-3} \text{ A} \\ &= 1.099 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{Voltage } V_{23456} &= IR_{23456} \\ &= 1.099 \times 10^{-3} \times \frac{131}{143} \times 1000 \\ &= 1.007 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Current } I_2 &= \frac{V_{23456}}{R_2} \\ &= \frac{1.007}{1 \times 10^3} = 1.007 \times 10^{-3} \text{ A} \\ &= 1.007 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{Current } I_{3456} &= \frac{V_{23456}}{R_{3456}} \\ &= \frac{1.007}{\frac{131}{12} \times 1000} \\ &= (9.22442 \times 10^{-5}) \text{ A} \\ &= 92.24 \text{ } \mu\text{A}\end{aligned}$$

(d2)

$$\begin{aligned}\text{Voltage } V_{456} &= I_{3456} \times R_{456} \\ &= 92.24 \times 10^{-6} \times \frac{11}{12} \times 1000 \\ &= 0.084553 \text{ V} \\ &= 84.56 \text{ mV}\end{aligned}$$

$$\begin{aligned}\text{Current } I_4 &= \frac{V_{456}}{R_4} \\ &= \frac{84.56 \times 10^{-3}}{1 \times 10^3} \\ &= 8.456 \times 10^{-5} \text{ A} \\ &= 84.56 \text{ } \mu\text{A}\end{aligned}$$

$$\begin{aligned}I_{56} &= \frac{V_{456}}{R_{56}} \\ &= \frac{84.56 \times 10^{-3}}{(1+10) \times 10^3} \\ &= 7.6872 \times 10^{-6} \text{ A} \\ &= 7.687 \text{ } \mu\text{A}\end{aligned}$$

$I_5 = I_6$ as they are in series connection.

$$\begin{aligned}\therefore V_6 &= I_6 \times R_6 \\ &= 7.687 \times 10^{-6} \times 1 \times 10^3 \\ &= 7.687 \times 10^{-3} \text{ V} = 7.687 \text{ mV}\end{aligned}$$

7 (1)

The hand calculation and the results using PSpice simulation are given below:

	Theoretical Calculation	PSpice Simulation result
V	12 V	12 V
I	1.099 mA	1.099 mA
V ₂₃₄₅₆	1.007 V	1.007 V
I ₂	1.007 mA	1.007 mA
I ₃₄₅₆	92.24 mA	92.25 mA
V ₄₅₆	84.56 mV	84.56 mV
I ₅	7.687 mA	7.687 mA
I ₆	7.687 mA	7.687 mA
V ₆	7.687 mV	7.687 mV


Questions and Answers:

- Using the recorded value of resistors, calculate the value of the currents and check if there is any discrepancies.
→ By using the recorded value of resistors, there is a small amount of

7(2)

discrepancies. The amount is very much little. The amount is less than 0.01%.

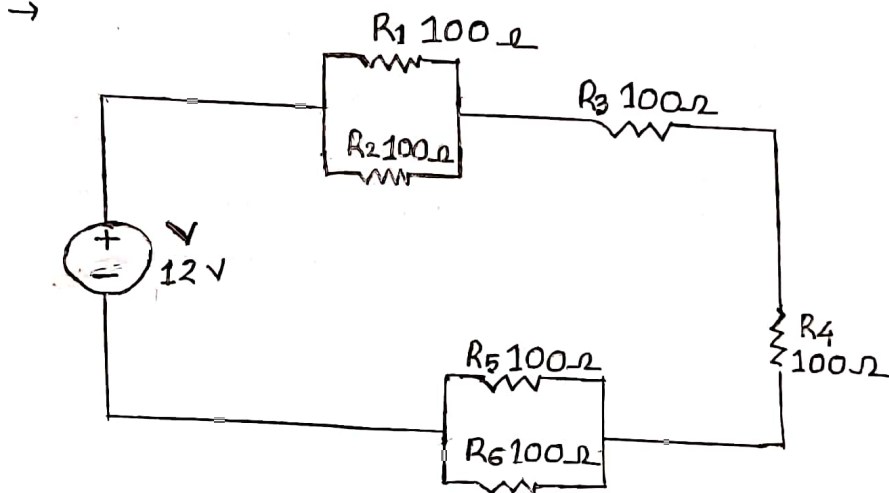2. You are given six 100 ohm resistors. Arrange these resistors as to provide an effective resistance value of 300 ohm.



Here, R_1 and R_2 are in Parallel:

$$\therefore R_{12} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{100 \times 100}{100 + 100} = 50\Omega$$

R_3 and R_4 are in series connection

$$R_{34} = R_3 + R_4 = 100 + 100 = 200\Omega$$

R_5 and R_6 are in parallel connection.

Here, R_1 and R_2 are in parallel connection

$$\therefore R_{12} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{100} + \frac{1}{100} \right)^{-1} \Omega$$

$$= 50 \Omega$$

R_5 and R_6 are also in parallel connection.

$$\therefore R_{56} = \left(\frac{1}{R_5} + \frac{1}{R_6} \right)^{-1} = \left(\frac{1}{100} + \frac{1}{100} \right)^{-1} \Omega$$

$$= 50 \Omega$$

R_{12} , R_3 , R_4 and R_{56} are in series connection.


$$\therefore \text{Total } R = (R_{12} + R_3 + R_4 + R_{56}) \Omega$$

$$= (50 + 100 + 100 + 50) \Omega$$

$$= 300 \Omega$$

3. You are given two $1.5 \text{ K}\Omega$ resistors and six $15 \text{ K}\Omega$ resistors. Arrange these resistors as to provide an effective resistance value of $3.25 \text{ K}\Omega$.

(1)

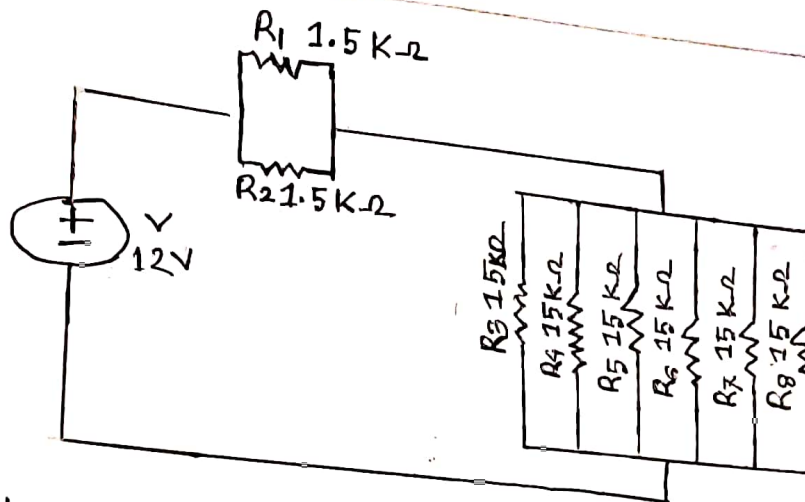

Here, R_1 and R_2 are in parallel connection:

$$\therefore R_{12} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{1.5} + \frac{1}{1.5} \right)^{-1} \text{ k}\Omega$$
$$= 0.75 \text{ k}\Omega$$

Here, R_3, R_4, R_5, R_6, R_7 and R_8 are in parallel connection:

$$\therefore R_{345678} = \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7} + \frac{1}{R_8} \right)^{-1}$$
$$= \left(\frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} \right)^{-1} \text{ k}\Omega$$
$$= 2.5 \text{ k}\Omega$$

$\therefore R_{12}$ and R_{345678} are in series connection.

$$\therefore \text{Total } R = R_{12} + R_{345678}$$
$$= (0.75 + 2.5) \text{ k}\Omega$$
$$= 3.25 \text{ k}\Omega$$

